Puzzle 1 Illuminate the LED without blowing it up!

Plug wires between the '+' power rail and the longest pin of the LED. The common anode supplies high voltage to all 3 colors.


Plug wires from each color to the '-' power rail to give a path for electrons to flow from 'GND'

Don't supply full power yet!

Using an adjustable power supply, slowly increase the voltage to around 2 or 3 volts to find out which color takes the least amount of power to illuminate. Any more will burn it out!


Unplug that color and turn the voltage up to 5 to see how much voltage it takes other colors to illuminate.

Use your multimeters to confirm!

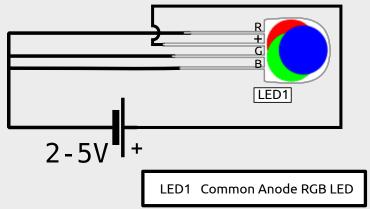

In order to illuminate 3 colors from the same power source, we can connect 'Resistors' of different values -- each resistor is made to give the flow of electrons a certain amount of extra work to do before flowing through, and is symbolized on the schematic with:

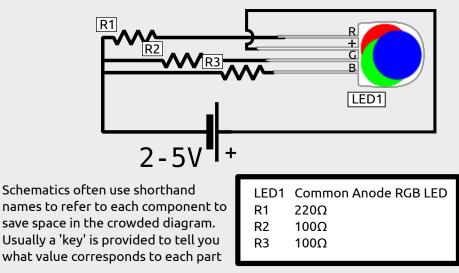Using a value of '220 ohms' will protect the color that needs the least amount of energy, while a lower resistance allows enough power to get to the other colors to shine bright.



A breadboard is designed to make it easier to try different combinations of parts without having to solder any wires together.

Each row, 1-30, has a small piece of metal underneath the holes. One connecting groups of 'a-b-c-d-e', and another connecting 'f-g-h-i-j'. You can bridge these sections with chips, resistors, and LEDs and have different amount of power on each side of the gap.

Outside of this middle-prototyping-area you get two 'power rails': supply power to + and - here and you'll never run out of places to connect to it.

